

EL203 Embedded Hardware Design

LAB_4

Aim: To perform different Tasks using Verilog HDL.

1. To design ALU using RTL and behavioral model. The input bits are of 4 bits. The ALU performs the following tasks:

- Arithmetic operations (addition, subtraction)
- Comparator operations (less than, equal to)
- Shifting operations (shift left, shift right)
- Bitwise operations (NAND and NOR logic)

Write test bench to check the functionality of ALU.

2. Design a 4-bit ripple carry adder in Verilog HDL. The module structure is as shown in Figure 1.

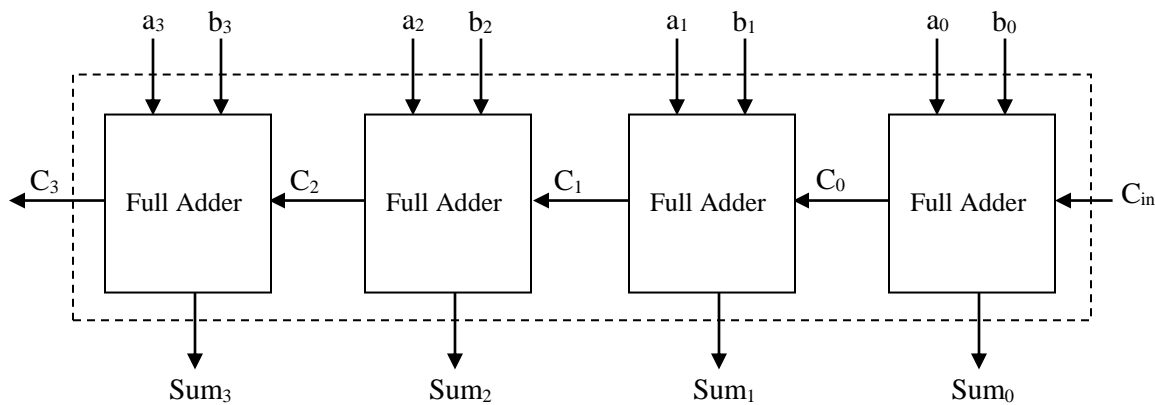


Figure 1: 4-bit ripple carry adder.

3. Design 2-input 4-bit BCD adder in Verilog HDL. Use 4-bit ripple carry adder as instance model for adder circuit in BCD adder.