

EL203 Embedded Hardware Design

LAB_6

Aim: To perform different Tasks using Verilog HDL.

1. (i) Design D Flip-flop
 - (a) With synchronous reset
 - (b) With asynchronous reset and preset with reset having highest priority
 - (ii) Write a test-bench to check functionality of the module in 1(i).
-
2. Generate clka, clkb, clkc pulses as shown in Fig. 1 using behavioral modeling (without using delay assignments).

 


Fig. 1. Clock signals.